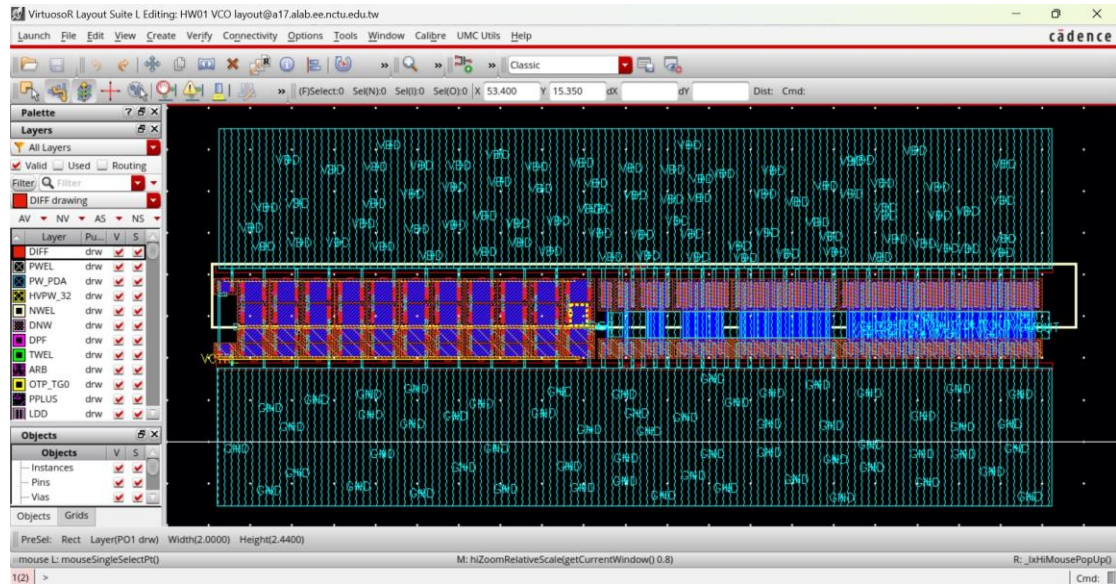


PMIC HW1_report


110511277 蔡東宏

1. Layout


11 級 oscillator+6 級 buffer




Oscillator:

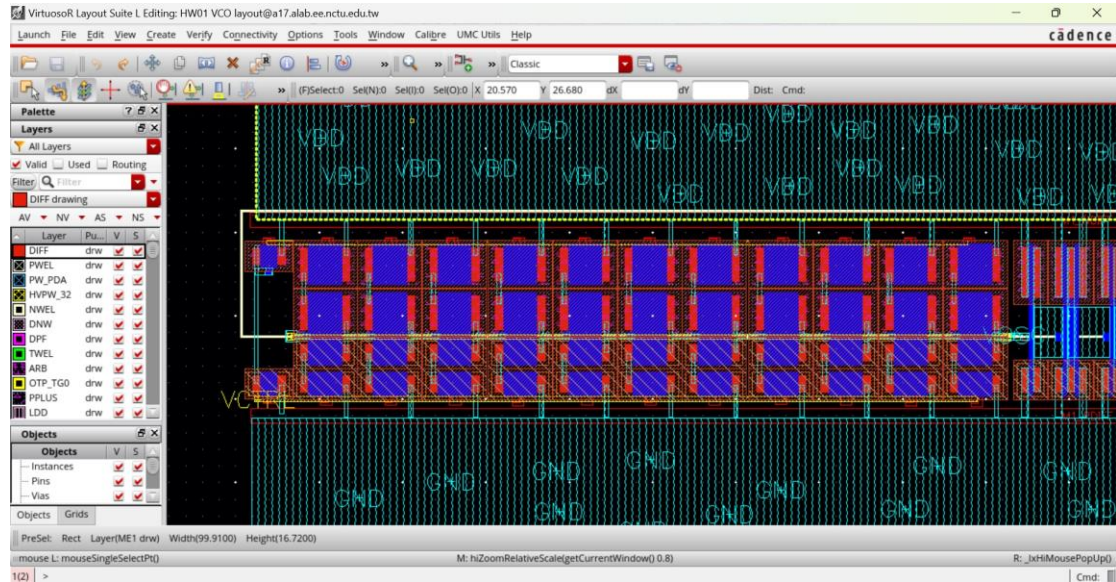


Buffer:

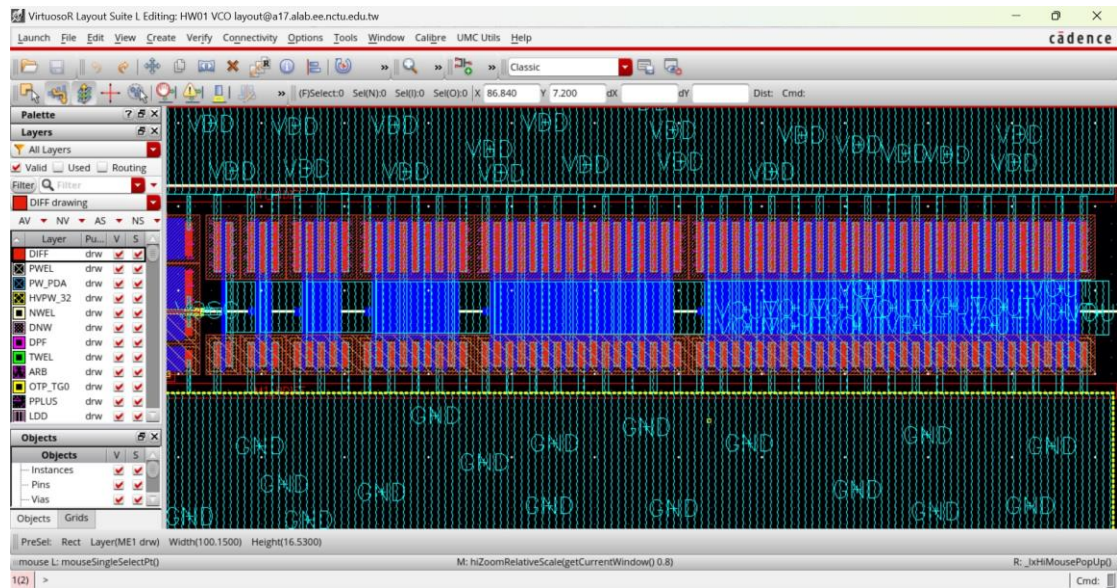

2. DRC

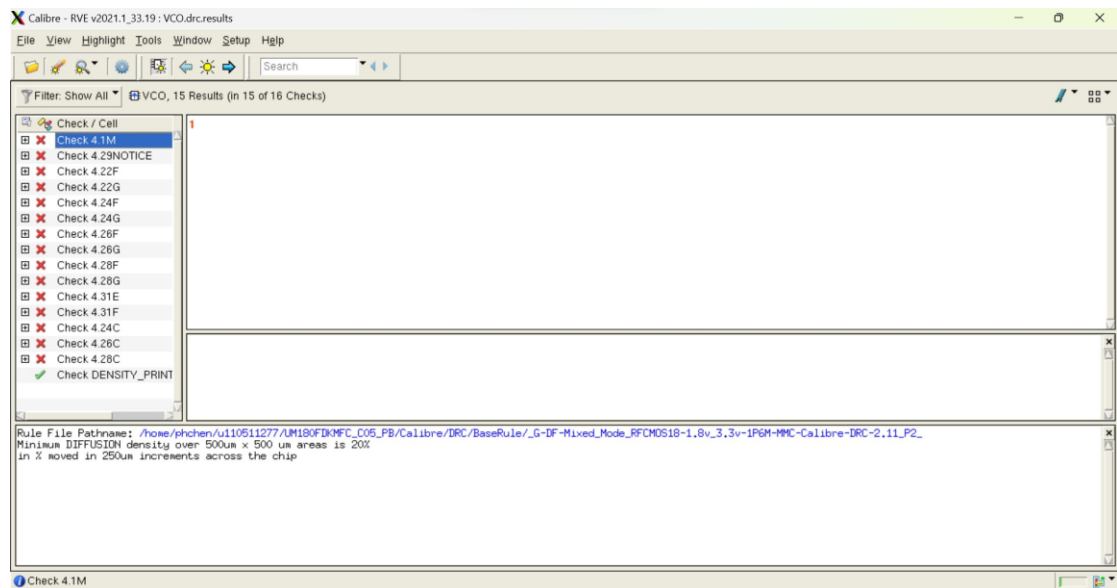


3. LVS

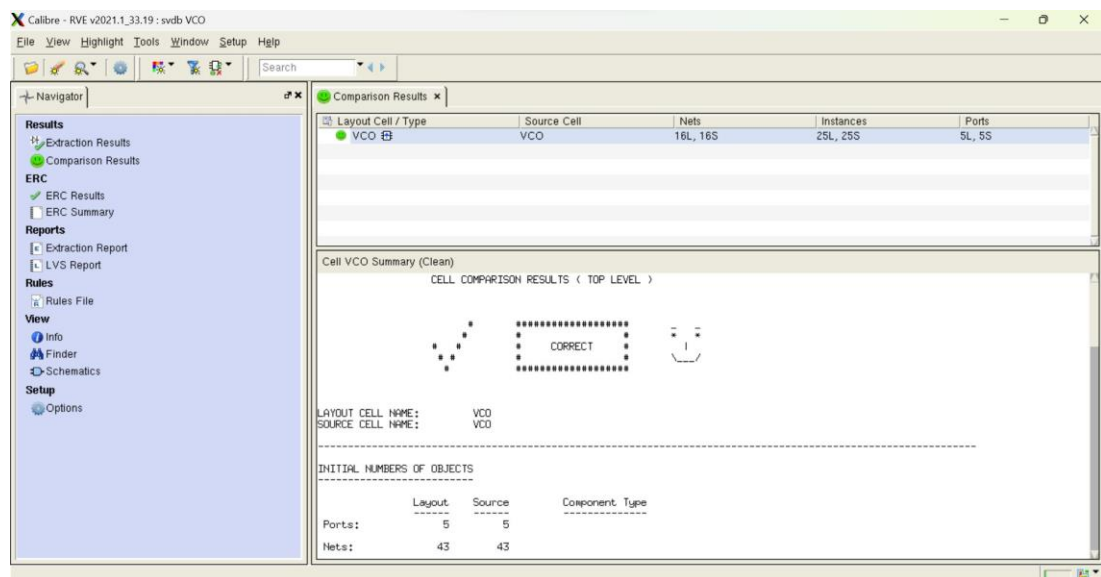


4. Result table

Parameter	Target	Pre-layout Simulation	Post-layout Simulation	Error Calculation
Supply Voltage (V_{DD})	1.8V	1.8 V	1.8 V	
Oscillation Range ($f_{min} \sim f_{max}$)	0.5MHz @ V_{CTRL}	495kHz @424mV	479.9kHz	3.05%
	2.5MHz @ V_{CTRL}	2.523MHz @548mV	2.444MHz	3.13%
Rising Time (t_F)	<0.5ns @0.5MHz	477.4ps	492.5ps	3.16%
	<0.5ns @2.5MHz	475.2ps	496.2ps	4.42%
Falling Time (t_R)	<0.5ns @0.5MHz	306.7ps	320.8ps	4.6%
	<0.5ns @2.5MHz	307ps	321.7ps	4.79%
Duty-cycle	47%<D<53%	51.1%	51.4%	
Number of Stage (N)	Any	11 级 OSC +	6 级 buffer	


Outcome(fmin) vctrl=424mV

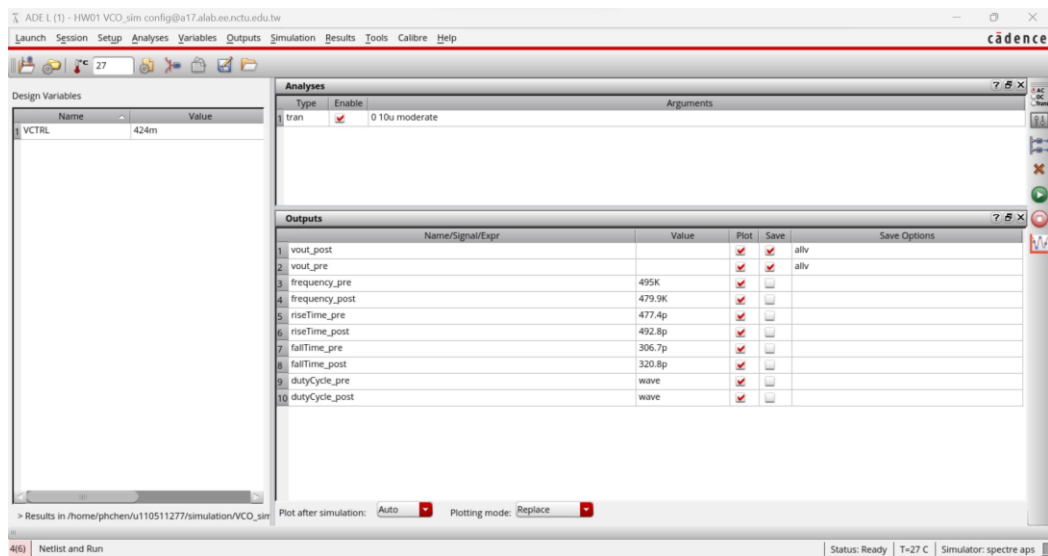


duty cycle(第一排為 pre-sim 第二排為 post-sim)

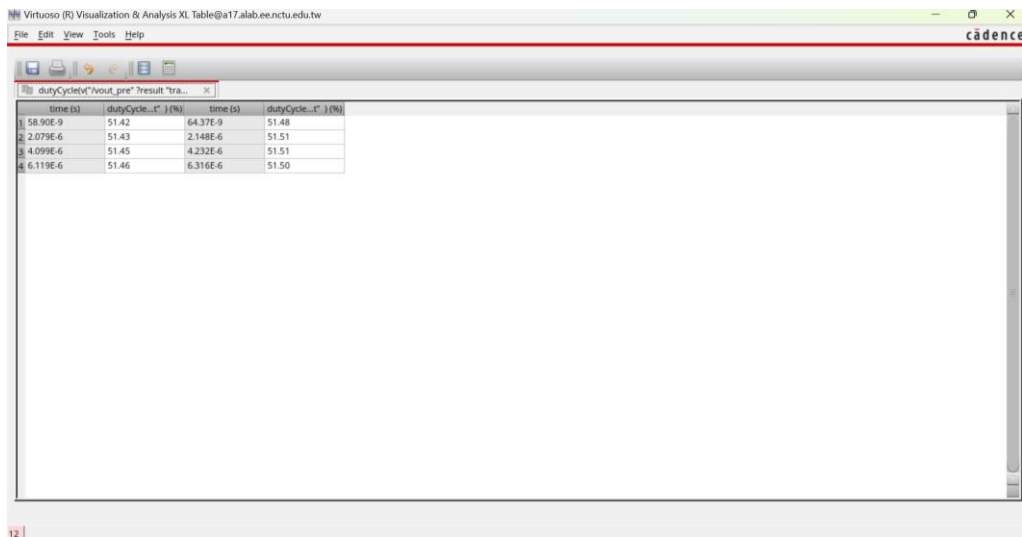

波形

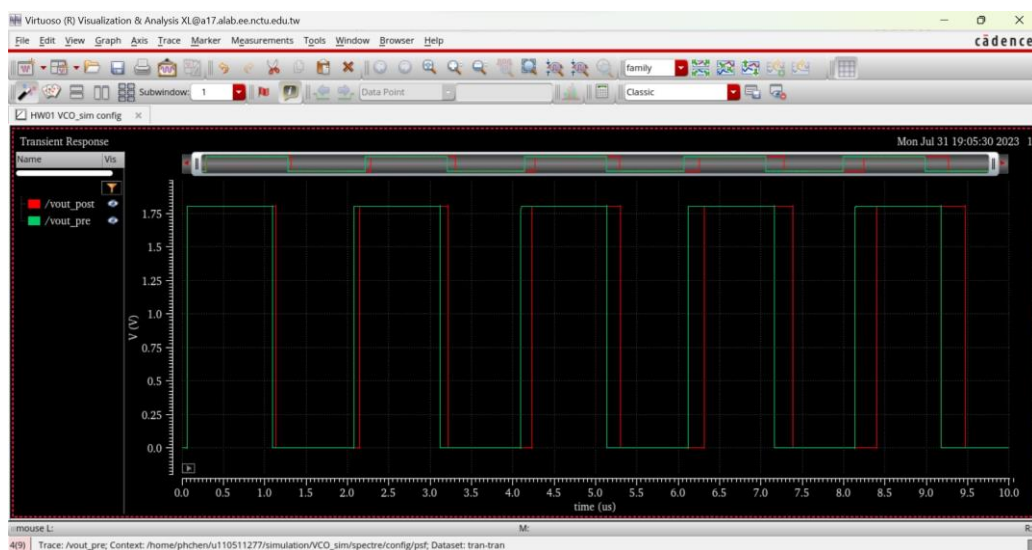

Outcome(fmax) vctrl=548mV

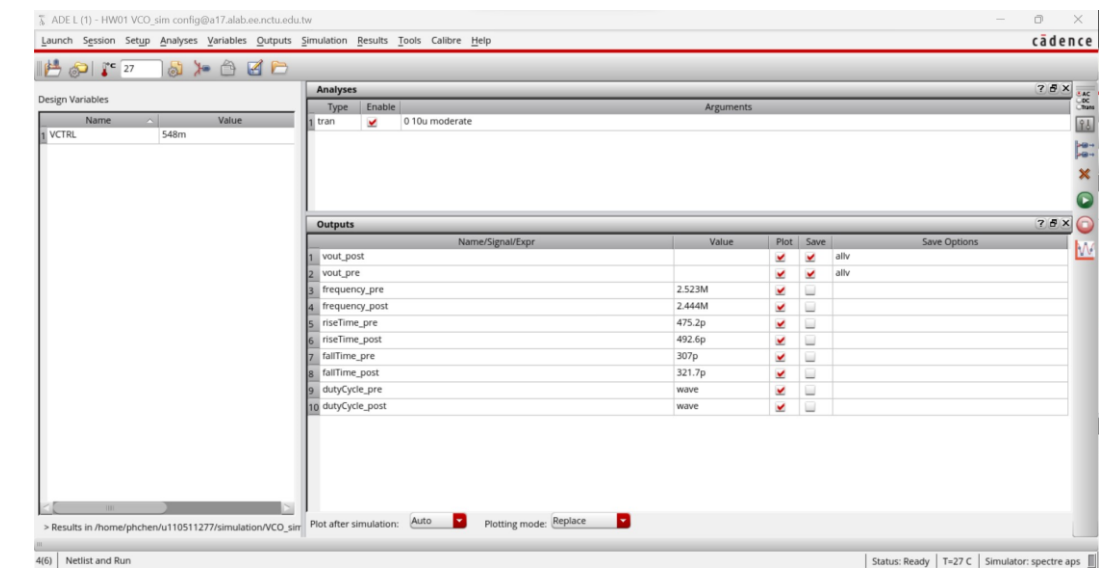

duty cycle(第一排為 pre-sim 第二排為 post-sim)

The screenshot displays a table of duty cycle data extracted from the simulation. The table has four columns: time (s), dutyCycle...t...) (%) for the pre-simulation, and time (s), dutyCycle...) (%) for the post-simulation. The data shows a series of measurements over time, with the duty cycle fluctuating between approximately 51.0% and 51.6%.

time (s)	dutyCycle...t...) (%)	time (s)	dutyCycle...) (%)
12.17E-9	51.10	4.923E-6	51.12
408.5E-9	51.11	13.36E-9	51.13
804.9E-9	51.09	6.150E-6	51.13
1.201E-6	51.10	6.559E-6	51.13
1.598E-6	51.11	3.695E-6	51.13
1.994E-6	51.09	5.332E-6	51.13
2.390E-6	51.10	2.468E-6	51.13
2.787E-6	51.11	831.5E-9	51.13
3.183E-6	51.10	6.968E-6	51.14
3.579E-6	51.09	422.3E-9	51.14
3.976E-6	51.11	9.423E-6	51.14
4.372E-6	51.10	7.787E-6	51.14
4.768E-6	51.09	1.241E-6	51.14
5.165E-6	51.10	8.196E-6	51.14
5.561E-6	51.10	4.104E-6	51.14
5.957E-6	51.09	1.650E-6	51.14
6.354E-6	51.11	2.877E-6	51.15
6.750E-6	51.10	2.059E-6	51.15
7.146E-6	51.08	7.378E-6	51.15
7.543E-6	51.10	5.741E-6	51.15
7.939E-6	51.10	9.014E-6	51.15
8.335E-6	51.09	3.286E-6	51.15
8.732E-6	51.10	4.514E-6	51.16
9.128E-6	51.11	8.605E-6	51.16
9.524E-6	51.10		

波形

The screenshot shows a transient response plot of the VCO output. The plot displays two square wave signals: vout_post (red) and vout_pre (green). The signals are periodic and have a high frequency. The x-axis represents time in microseconds (us), ranging from 0.0 to 4.4. The y-axis represents voltage in Volts (V), ranging from 0.0 to 1.75. The plot is titled 'Transient Response' and includes a legend for the signals.

Transient Response

Mon Jul 31 19:09:02 2023

V (V)

time (us)